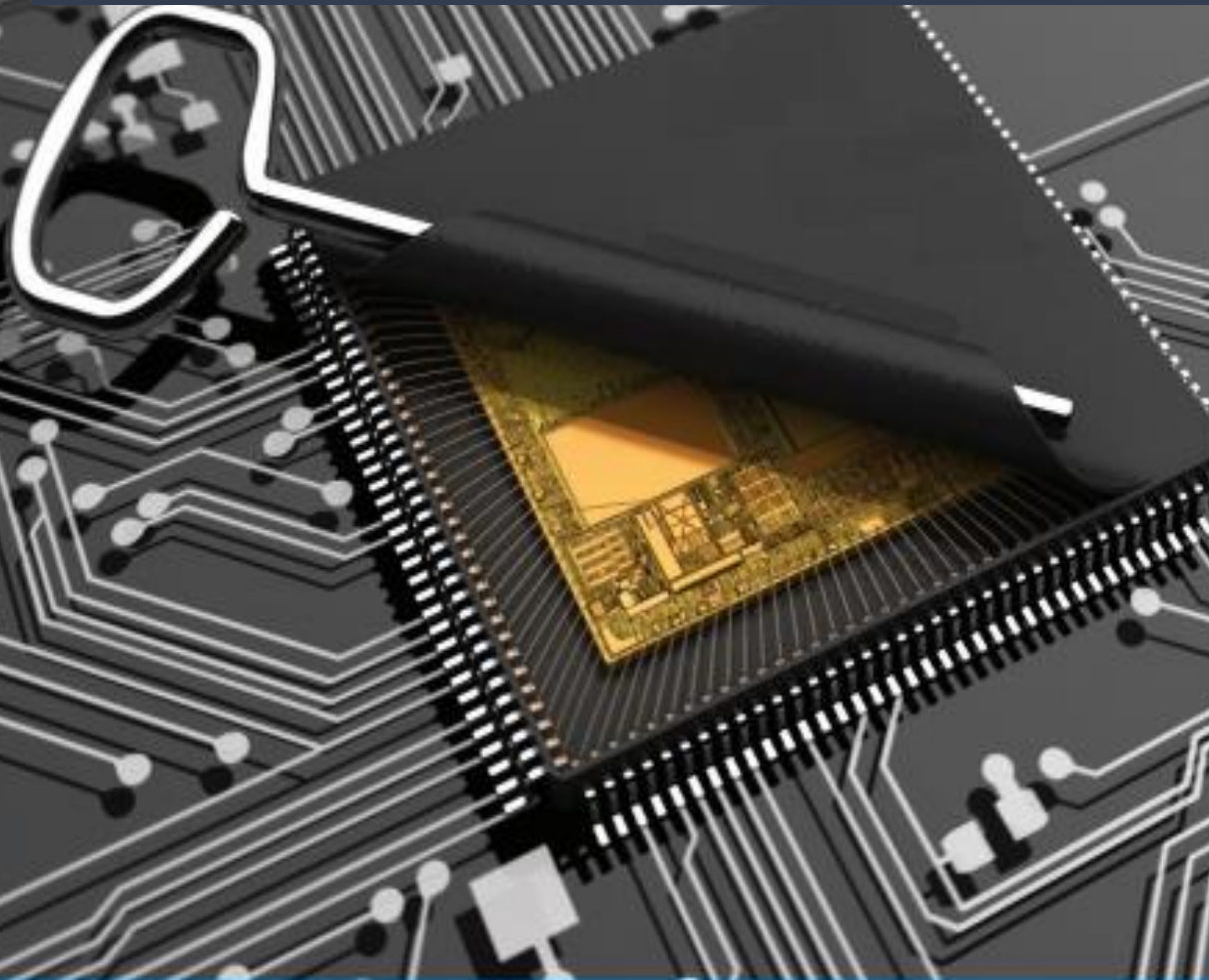


Keypad Interfacing

with 8086

Made Simple

By Obed Mokweri



Contents;



- i) Keypad Layout
- ii) The Logic
- iii) Programming




Embedded Systems


Compiled by:
Eng. Obed © 2018
(Embedded Systems
Developer)

Keypad Layout


Keypad Layout

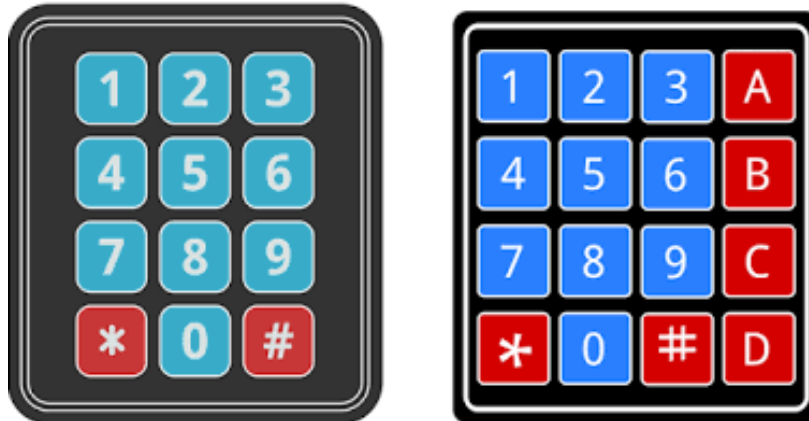

Typical Matrix Keypads

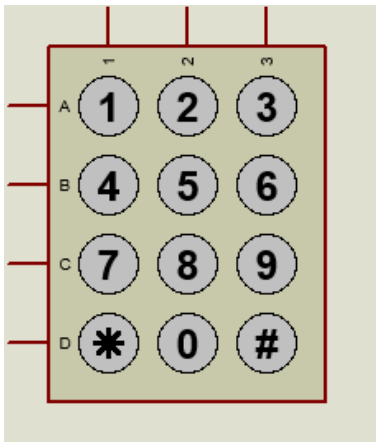

Keypad Symbol for Proteus

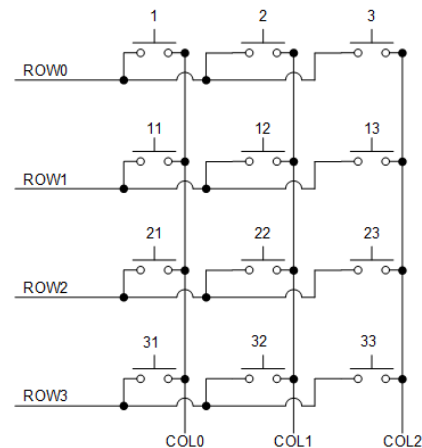

4x3 Matrix Keypad Layout

Brief Description;

A matrix keypad consists of arrangement of switches in matrix format in rows and columns with the microprocessor I/O pins connected to the rows and columns of the matrix such that switches in each row are connected to one pin and switches in each column are connected to another pin.

A keypad is generally a matrix arrangement of tact switches which are basically push button switches.

The Logic

How a Matrix Keypad works:


There are numerous techniques depending on the connection keypad with microcontroller, but the fundamental logic making the columns as inputs and drive the rows making them as output. So as to detect which key is pressed from the matrix keypad, the row lines are to be made low one by one and read the columns.

Here we are going to use a 4×3 matrix keypad. It is 12 keys keypad consists of four rows and three columns. Assume that if row1 is made low, then read the columns. If any of the key in row1 is pressed then correspondingly the column 1 will give low that is if second key is pressed in row1, then column2 will give low. Suppose, if we press **1** on keypad then **switch 1** (on Figure on page above) are switched ON makes the connection and outputs the value through the microprocessor. Similarly, all keys will perform same operation as key 1. We cannot press two keys at the same time. There should be a time difference between to press the key with one other.

Logic sequence:


Step 1:

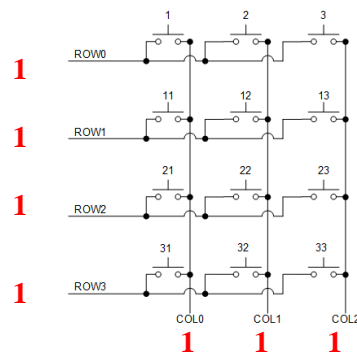The first step involved in interfacing the matrix keypad is to write all logic 1's to the rows and all logic 1's to the columns. This indicates no key pressed. Remember, the row pins are inputs and column pins, outputs.




Step 2:

Then let's set column 0 **LOW**.

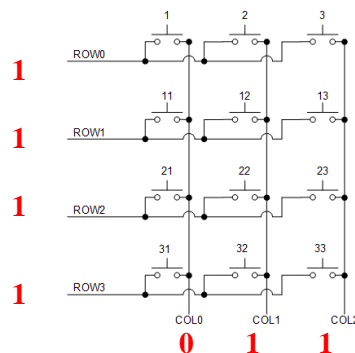


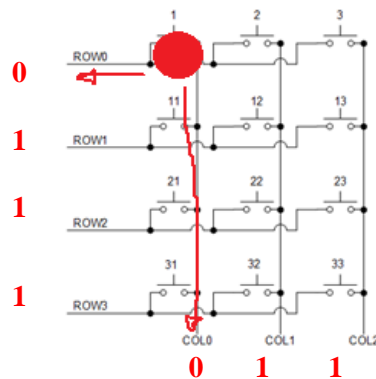Now, we loop through the rows in the column to check if any key is pressed. If say key 1 is pressed, then the value of row 0 goes LOW.



By checking the value on the row pins, then we can tell which key is pressed. We then output the value of the key pressed to another port or use however we want. That's sounds easy, right? I think so.

Also if Key 8 is pressed;

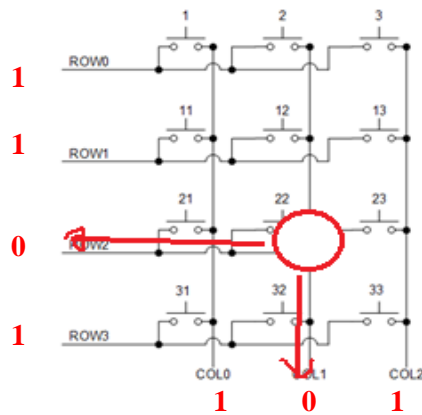

That's what happens for all the columns and pins. The program code will fully illustrate this concept.


Programming

Sample Application

A typical application of the keypad is entry of values to a system. To illustrate this, we shall use a seven-segment display to display the key pressed on the keypad. This can also be done with an LCD but since we have not handled LCD interfacing, I prefer simpler concepts first. Oh, am not sure if myself I remember how the segment display works and I will refresh and attach it as an appendix.

Circuit Diagram

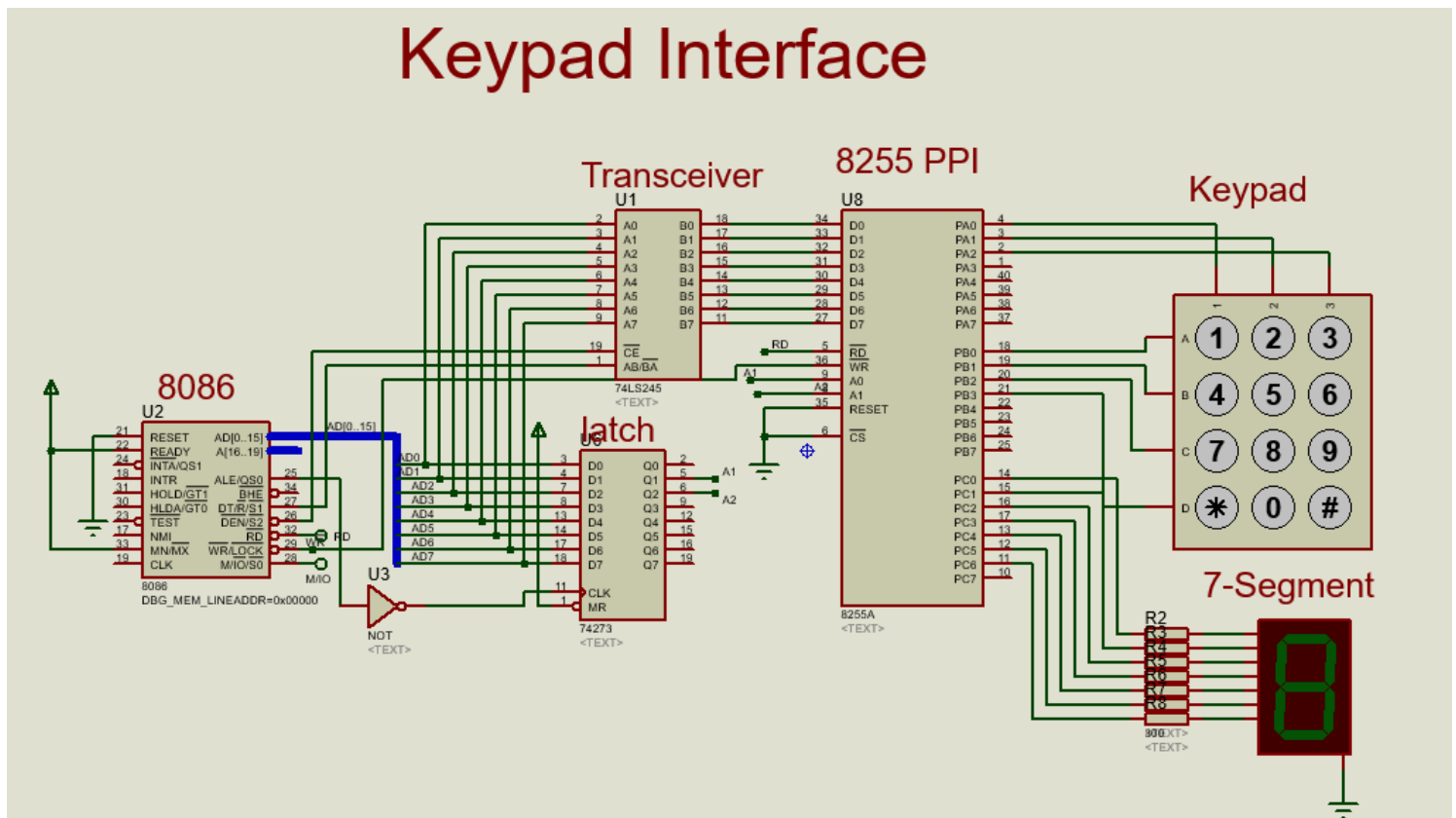The circuit for this application was done in Proteus.



Assembly Code

```
001
002
003 data segment ; Define Ports of 8255
004
005 PORTA EQU 00H
006 PORTB EQU 02H
007 PORTC EQU 04H
008 PCW EQU 06H
009
010 ends
011
012 stack segment
013 dw 128 dup(0)
014 ends
015
016 code segment
017 start:
018
019 mov ax, data ; Move data to ax
020 mov ds, ax ; fill ds with ax
021 mov es, ax ; fill es with ax
022 mov dx, PCW ; enter PWC to DX
023
024 mov al, 10000010B ; Control Word-Mode 1 PORTA as output, PORTB input
025 out dx, al ; give this mode to IC I/O
026
027 Main:
028 mov cx, 00FFH ; fill in the value of cx with 00ffh
029 mov al, 0FEH ; value = 1111 1110, set column 0 low
030 mov dx, PORTA ; mov PORTA to DX
031 out dx, al ; Give this value to PORTA
032
033 COLUMN0:
034 ; Check ROW0
035 in al, PORTB ; Get PORTB value
036
037 cmp al, 0FEH ; If PORTB = 1111 1110 - button 1 keypad is pressed?
038 jne row1 ; If not, go to ROW1
039 mov al, 006H ; If so, give PORC 006H or 7-Segment value to PORTC
040 out portc, al ; Turning on number 1
041 jmp go ; continue loop
042
043 row1: cmp al, 0FDH ; Is PORTB == 1111 1101 or (4) keypad button pressed?
044 jne row2 ; If not, go to ROW2 of column 1
045 mov al, 066H ; If so, give PORC 066H or 7-Segment to PORTC
046 out portc, al ; Turn on the number 4
047 jmp go ; continue loop
048
049 row2:
050 cmp al, 0FBH ; Is PORTB worth 0FBH or 7 Keypad button pressed?
051 jne row3 ; If not, go to ROW3
052 mov al, 007H ; If so, give PORC 007H or 7-Segment value to PORTC
053 out portc, al ; Turning on the number 7
054 jmp go ; Go to GO
055
056 row3:
057 cmp al, 0F7H ; Is PORTB == 0F7H or keypad star button pressed?
058 jne go ; continue loop
059 mov al, 07CH ; If so, give PORC value 07CH or 7-Segment to PORTC
060 out portc, al ; Turn on the letters b
061
062 GO:
063 loop column0 ; Looping to COLUMN1 is CX
064
065 mov cx, 00FFH ; Initialize counter
066 mov al, 0FDH ; value = 1111 1101, set column 1 low
067 mov dx, PORTA ; enter PORTA to DX
068 out dx, al ; Give this value to PORTA
069
070 COLUMN1:
071
072 in al, PORTB ; Get PORTB value
073 cmp al, 0FEH ; Is PORTB == 0FEH or 2 Keypad button pressed?
074 jne row11 ; If not, go to ROW12
075 mov al, 05BH ; If so, give PORC 05BH or 7-Segment to PORTC
076 out portc, al ; Turn on the number 2
077 jmp go2 ; Go to GO2
```



```

078      ROW11:  CMP AL,0FDH      ; Is PORTB == 0FDH or 5 Keypad button pressed?
079      JNE ROW21                ; If not, go to ROW22
080      MOV AL,06DH;             ; If so, give PORC 06DH or 7-Segment to PORTC
081      OUT PORTC,AL;           ; Turn 5 on
082      JMP GO2
083
084      ROW21:
085      CMP AL,0FBH              ; Is PORTB == 0FBH or keypad 8 keypad being pressed?
086      JNE ROW31                ; If not, go to ROW32
087      MOV AL,07FH;             ; If so, give PORC 07FH or 7-Segment to PORTC
088      OUT PORTC,AL;           ; Turn on the number 8
089      JMP GO2                  ; continue loop
090
091      ROW31:
092      CMP AL,0F7H              ; Is PORTB == 0F7H or keypad 0 keypad being pressed?
093      JNE GO2                  ; If not, go to GO2
094      MOV AL,03FH;             ; If so, give PORC 03FH or 7-Segment value to PORTC
095      OUT PORTC,AL;           ; Turns 0 on
096
097      GO2:
098      LOOP COLUMN1             ; Looping to COLUMN2 is CX
099
100      MOV CX,00FFH             ; fill in the value of CX with 00ffh
101      MOV AL,0FBH              ; value = 1111 1011, set column 2 low
102      MOV DX,PORTA             ; enter PORTA to DX
103      OUT DX,AL                ; Give this value to PORTA
104
105      COLUMN2:
106
107      IN AL,PORTB               ; Get PORTB value
108      CMP AL,0FEH              ; Is PORTB == 0FEH or button 3 keypad is pressed?
109      JNE ROW12                ; If not, go to ROW13
110      MOV AL,04FH;             ; If so, give PORC 04FH or 7-Segment value to PORTC
111      OUT PORTC,AL;           ; Turn on the number 3
112      JMP GO3                  ; Continue loop
113
114      ROW12:  CMP AL,0FDH      ; Is PORTB == 0FDH or 6 Keypad button pressed?
115      JNE ROW22                ; If not, go to ROW23
116      MOV AL,07DH;             ; If so, give PORC 07DH or 7-Segment to PORTCrgi to ROW23
117      OUT PORTC,AL;           ; Turn on the number 6
118      JMP GO3                  ; continue loop
119
120      ROW22:
121      CMP AL,0FBH              ; Is PORTB == 0FBH or keypad 9 key pressed?
122      JNE ROW32                ; If not, go to ROW33
123      MOV AL,06FH;             ; If so, give PORC 06FH or 7-Segment to PORTC
124      OUT PORTC,AL;           ; Turning on the number 9
125      JMP GO3                  ; Continue loop
126
127      ROW32:
128      CMP AL,0F7H              ; Is PORTB == 0F7H or Keypad Fence button pressed?
129      JNE GO3                  ; If not, go to GO3
130      MOV AL,00CH;             ; If so, give PORC 00CH or 7-Segment value to PORTC
131      OUT PORTC,AL;           ; Turn on the letter A
132
133      GO3:
134      LOOP COLUMN2             ; Looping to COLUMN2 by CX
135      JMP Main                  ; Repeat the program again
136
137
138      |
139      end start
140

```

Quite a lengthy code, yes? Not really.



You remember how to generate the executable file for use in Proteus? I hope you do.

I simulated mine and oh yees, it worked.

By the way, this nice quote "If it works, its obsolete". We should now do something else much better.

Appendix:


Seven Segment Display

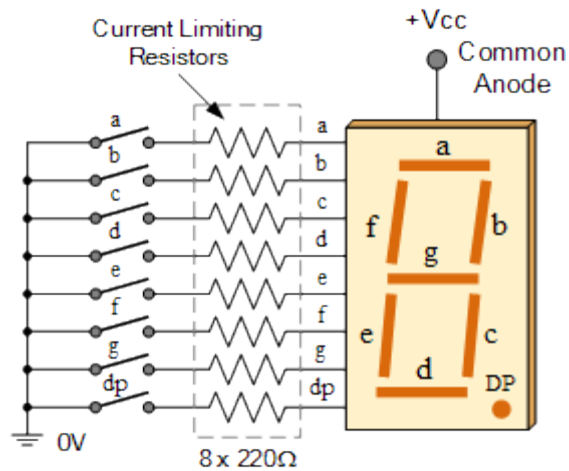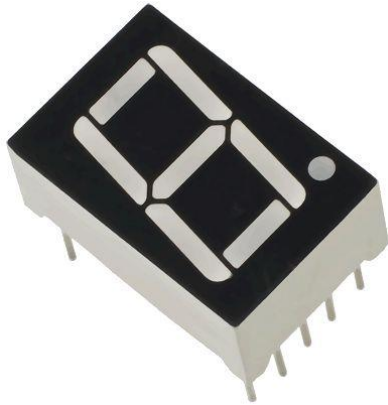

How it Works;

As shown in the above images of a 7-segment display, it consists of 8 LEDs, each LED used to illuminate one segment of unit and the 8th LED used to illuminate DOT in 7 segment display. We can refer each segment as a LINE, as we can see there are 7 lines in the unit, which are used to display a number/character. We can refer each segment "a,b,c,d,e,f,g" and for dot character we will use "h". There are 10 pins, in which 8 pins are used to refer a,b,c,d,e,f,g and h/dp, the two middle pins are common anode/cathode of all the LEDs. These common anode/cathodes are internally shorted so we need to connect only one COM pin.

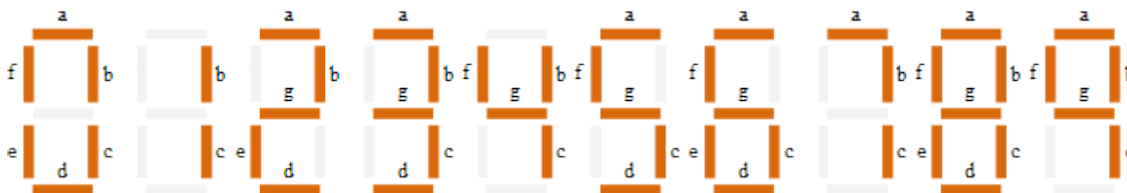7-Segment Display Segments for all Numbers.



Then for a 7-segment display, we can produce a truth table giving the individual segments that need to be illuminated in order to produce the required decimal digit from 0 through 9 as shown below.

Digit to Display	h g f e d c b a	Hex code
0	00111111	3F
1	11111001	F9
2	01011011	5B
3	01001111	4F
4	01100110	66
5	01101101	6D
6	01111101	7D
7	00000111	07
8	01111111	7F
9	01101111	6F

References;

<https://www.elprocus.com/matrix-keypad-interfacing-with-microcontroller/>

http://pcbheaven.com/wikipages/How_Key_Matrices_Works/

<https://circuitdigest.com/microcontroller-projects/keypad-interfacing-with-avr-atmega32>

<https://embedjournal.com/interface-4x4-matrix-keypad-with-microcontroller/>

<https://www.electronics-tutorials.ws/blog/7-segment-display-tutorial.html>

<https://circuitdigest.com/article/7-segment-display>

NOTE: This document and its accompanying files are also available for download in [Github](#), a tool I recommend to you guys. The particular link will be provided.

Look forward to the next document release. I will always share any good stuff I manage to chew as long as God gives breathe. Should you find any challenges, I would be glad to help or we can Google it together. But always try finding a solution yourself first.

mogsobd@gmail.com

NEXT Release: LCD Interface

HAVE FUN MEMBERS!!!!